

2008년 국가직 7급 회로이론 봉책형 해설

01. ①	02. ④	03. ①	04. ③	05. ②	06. ②	07. ②	08. ③	09. ①	10. ②
11. ③	12. ④	13. ④	14. ①	15. ③	16. ②	17. ②	18. ④	19. ④	20. ①

1. 【정답】 ①

$$Z_{TH} = \frac{6(-j2)}{6-j2} = \frac{-j6}{3-j} = \frac{-j6(3+j)}{10} = 0.6 - j1.8 [\Omega]$$

$$V_{TH} = 20 \angle 0^\circ \times \frac{-j2}{6-j2} = 20 \times \frac{-j}{3-j} = 20 \times \frac{-j(3+j)}{10} = -2j(3+j)$$

$$V_{TH} = 2 - j6 [V]$$

2. 【정답】 ④

$$\frac{V_1}{3} + \frac{V_2}{3} + \dots + \frac{V_{100}}{3} = \frac{0 - V_o}{2}$$

$$\frac{1}{3}(V_1 + V_2 + \dots + V_{100}) = -\frac{V_o}{2}$$

$$V_o = -\frac{2}{3} \times \frac{100 \times 101}{2} = -\frac{10100}{3} [mV]$$

3. 【정답】 ①

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{4I_1}{I_1} = 4, \quad Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{I_2}{I_2} = 1$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{I_1}{I_1} = 1, \quad Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{(s+1)I_2}{I_2} = s+1$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 4 & 1 \\ 1 & (s+1) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

4. 【정답】 ③

$$10u(t) = \frac{dI}{dt} + V_c + 3I, \text{ 라플라스 변환하면 } \frac{10}{s} = sI(s) + V_c(s) + 3I(s)$$

$$I = \frac{1}{2} \frac{dV_c}{dt}, \text{ 라플라스 변환하면 } I(s) = \frac{1}{2}(sV_c(s) - 5), \quad V_c(s) = \frac{2I(s) + 5}{s}$$

$$\frac{10}{s} = (s+3)I(s) + \frac{2I(s) + 5}{s}$$

$$I(s) = \frac{\frac{5}{s}}{s+3+\frac{2}{s}} = \frac{5}{s^2+3s+2} = \frac{5}{(s+1)(s+2)} = 5\left(\frac{1}{s+1} - \frac{1}{s+2}\right)$$

역변환하면 $I(t) = 5e^{-t} - 5e^{-2t}$, $t \geq 0$

5. 【정답】 ②

$$V_2(s) = -4sI_1(s)$$

$$I_1(s) = \frac{V_1(s)}{6+2s}$$

$$\frac{V_2(s)}{V_1(s)} = \frac{-4s}{2s+6}$$

6. 【정답】 ②

$$\frac{V_1}{R_1} + g_m V_1 + \frac{V_{in}}{R_{in}} = \frac{V_{in}}{R_2}$$

$$V_1 = -V_{in}$$

$$\frac{-V_{in}}{R_1} - g_m V_{in} + \frac{V_{in}}{R_{in}} = \frac{V_{in}}{R_2}$$

$$-\frac{1}{R_1} - g_m + \frac{1}{R_{in}} = \frac{1}{R_2}, \quad \frac{1}{R_{in}} = \frac{1}{R_1} + \frac{1}{R_2} + g_m$$

$$R_{in} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + g_m} = \frac{R_1 R_2}{R_1 + R_2 + g_m R_1 R_2}$$

7. 【정답】 ②

$$V_a = 0 \text{ [V]} \text{로 놓으면 } V_c = 4 \times 3 = 12 \text{ [V]}$$

$$\frac{12-4}{8} = \frac{4-0}{R_1}, \quad R_1 = 4 \text{ [k}\Omega\text{]}$$

8. 【정답】 ③

$$V(t) = u(t) - u(t-0.1)$$

$$V(s) = \frac{1}{s}(1 - e^{-0.1s})$$

$$I(s) = \frac{V(s)}{R + \frac{1}{sC}} = \frac{sC}{sCR + 1} V(s)$$

$$CR = 0.1 \times 10^{-6} \times 3 \times 10^6 = 0.3$$

$$I(s) = \frac{10^{-7}s}{0.3s+1} \cdot \frac{1}{s}(1 - e^{-0.1s}) = \frac{10^{-7}}{0.3s+1}(1 - e^{-0.1s})$$

$$I(s) = \frac{\frac{10^{-7}}{0.3}}{s + \frac{10}{3}}(1 - e^{-0.1s}) = \frac{1}{3} \frac{1}{s + \frac{10}{3}}(1 - e^{-0.1s}) 10^{-6}$$

$$I(t) = \frac{1}{3} \left(e^{-\frac{10}{3}t} - e^{-\frac{10}{3}(t-0.1)} u(t-0.1) \right) = \frac{1}{3} e^{-\frac{10}{3}t} \left(1 - e^{\frac{1}{3}} u(t-0.1) \right) [\mu A]$$

$$I(0.2) = \frac{1}{3} e^{-\frac{2}{3}} \left(1 - e^{\frac{1}{3}} \right) = -\frac{1}{3} e^{-\frac{2}{3}} \left(e^{\frac{1}{3}} - 1 \right) = -\frac{1}{3} \left(1 - e^{-\frac{1}{3}} \right) e^{-\frac{1}{3}} [\mu A]$$

다른 풀이

$0 \leq t < 0.1$ 에서 $V(s) = \frac{1}{s}$ 이므로

$$I_1(s) = \frac{C}{sCR+1} = \frac{10^{-7}}{0.3s+1} = \frac{1}{3} \frac{1}{s + \frac{10}{3}} 10^{-6}$$

$$I_1(t) = \frac{1}{3} e^{-\frac{10}{3}t} [\mu A]$$

$t \geq 0.1$ 일 때는 $-u(t-0.1)$ 의 입력이 추가된 것으로 볼 수 있으므로

$$I_2(t) = -\frac{1}{3} e^{-\frac{10}{3}(t-0.1)} [\mu A]$$

$$I(t) = I_1(t) + I_2(t) = \frac{1}{3} e^{-\frac{10}{3}t} - \frac{1}{3} e^{-\frac{10}{3}(t-0.1)} [\mu A]$$

$$I(0.2) = \frac{1}{3} e^{-\frac{2}{3}} - \frac{1}{3} e^{-\frac{1}{3}} = -\frac{1}{3} \left(1 - e^{-\frac{1}{3}} \right) e^{-\frac{1}{3}} [\mu A]$$

9. 【정답】 ①

$$v_L = L \frac{di}{dt} \text{에서 라플라스 변환하면 } V_L(s) = LsI(s) - LI(0)$$

$$i = C \frac{dV}{dt} \text{에서 라플라스 변환하면 } I(s) = CsV(s) - CV(0), \quad V(s) \text{에 관하여 정리하면}$$

$$V(s) = \frac{I(s)}{sC} + \frac{V(0)}{s}$$

따라서 변환회로로 옳은 것은 ①번이다.

10. 【정답】 ②

문제의 신호는 기함수이므로 푸리에 계수 중 b_n 만 구하면 된다.

$$b_n = \frac{2}{T_0} \left[\int_{-T_0/2}^{T_0/2} \frac{2\pi}{T_0} t \sin n \frac{2\pi}{T_0} t dt \right]$$

+	$\frac{2\pi}{T_0} t$	$\sin \frac{2n\pi}{T_0} t$
-	$\frac{2\pi}{T_0}$	$-\frac{T_0}{2n\pi} \cos \frac{2n\pi}{T_0} t$
+	0	$-\left(\frac{T_0}{2n\pi}\right)^2 \sin \frac{2n\pi}{T_0} t$

$$b_n = \frac{2}{T_0} \left[-\frac{t}{n} \cos \frac{2n\pi}{T_0} t + \frac{T_0}{2n^2\pi} \sin \frac{2n\pi}{T_0} t \right]_{-T_0/2}^{T_0/2}$$

$$b_n = \frac{2}{T_0} \left(-\frac{T_0}{2n} \cos n\pi - \left(\frac{T_0}{2n} \cos n\pi \right) \right) = -\frac{2}{n} \cos n\pi$$

$$b_1 = 2, \quad b_2 = -1, \quad b_3 = \frac{2}{3}, \quad b_4 = -\frac{1}{2}, \quad \dots$$

$$V_i(t) = 2 \sin \frac{2\pi}{T_0} t - \sin \frac{4\pi}{T_0} t + \frac{2}{3} \sin \frac{6\pi}{T_0} t - \frac{1}{2} \sin \frac{8\pi}{T_0} t + \dots$$

차단 각주파수가 $\frac{7\pi}{T_0}$ 인 이상적인 저역통과 필터이므로 $\frac{7\pi}{T_0}$ 보다 작은 주파수만 통과시킨다.

$$\text{따라서 } V_o(t) = 2 \sin \frac{2\pi}{T_0} t - \sin \frac{4\pi}{T_0} t + \frac{2}{3} \sin \frac{6\pi}{T_0} t$$

$$\text{실효값은 } \sqrt{\left(\frac{2}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{2}{3\sqrt{2}}\right)^2} = \sqrt{2 + \frac{1}{2} + \frac{2}{9}} = \sqrt{\frac{49}{18}} = \frac{7}{3\sqrt{2}} = \frac{7}{6} \sqrt{2}$$

11. 【정답】 ③

③ 대역통과필터 : $N(s) = a_1 s$

12. 【정답】 ④

$$A = \frac{V_1}{V_2} \bigg|_{I_2=0} = \frac{2 + \frac{1}{j\omega}}{\frac{1}{j\omega}} = 1 + 2j\omega$$

13. 【정답】 ④

$$\text{무손실 전송선로에서 } Z_{\text{in}} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$

종단이 단락되었으므로 부하 임피던스 $Z_L = 0$ 이고, $\beta = \frac{2\pi}{\lambda}$, $l = \frac{\lambda}{6}$ 이다.

$$j40\sqrt{3} = jZ_0 \tan\left(\frac{2\pi}{\lambda} \times \frac{\lambda}{6}\right) = jZ_0 \tan \frac{\pi}{3}$$

$$Z_0 = 40 [\Omega]$$

14. 【정답】 ①

$$\text{왼쪽 그림에서 } V_1 - KV_1 = \frac{I}{Y}$$

$$\text{오른쪽 그림에서 } V_1 = \frac{I}{Y_1}, KV_1 = -\frac{I}{Y_2}$$

$$V_1 = \frac{I}{Y(1-K)} \text{이므로 } \frac{I}{Y(1-K)} = \frac{I}{Y_1}, \frac{KI}{Y(1-K)} = -\frac{I}{Y_2}$$

$$Y_1 = (1-K)Y, Y_2 = \left(\frac{K-1}{K}\right)Y = \left(1 - \frac{1}{K}\right)Y$$

15. 【정답】 ③

$$\text{① 전달함수는 } \frac{V_1 - 0}{R_1} = \frac{0 - V_2}{R_2 + \frac{1}{sC}} \text{에서 } \frac{V_2}{V_1} = -\left(\frac{R_2}{R_1} + \frac{1}{sCR_1}\right) \text{이다.}$$

$$\text{② } V_2(s) = -\frac{R_2}{R_1} V_1(s) - \frac{1}{sCR_1} V_1(s) \text{에서 역변환하면}$$

$$V_2(t) = -\frac{R_2}{R_1} V_1(t) - \frac{1}{CR_1} \int_0^{t_1} V_1(\tau) d\tau \text{ 이다. (단, } C \text{의 초기전압은 } 0 \text{으로 가정한다.)}$$

$$\text{③ } \frac{V_2}{V_1} = -\frac{sCR_2 + 1}{sCR_1} \text{이므로 극점(pole)은 } s = 0, \text{ 영점(zero)은 } s = -\frac{1}{CR_2} \text{이다.}$$

극점(pole)과 영점(zero)은 각각 한 개가 있다.

④ 직류에서 커패시터는 개방회로로 작동하므로 저항이 무한대(∞)이다.

$$\frac{V_1 - 0}{R_1} = \frac{0 - V_2}{\infty} \text{에서 } \frac{V_2}{V_1} = -\frac{\infty}{R_2} = -\infty \text{이므로 전압이득은 무한대이다.}$$

16. 【정답】 ②

$$\frac{V_s(t) - V(t)}{3} + 0.2 \frac{d(V_s(t) - V(t))}{dt} = 0.3 \frac{dV(t)}{dt} + I(t)$$

$$V(t) = 2I(t) + 0.2 \frac{dI(t)}{dt}$$

$$\frac{dI(t)}{dt} = -10I(t) + 5V(t)$$

$$0.5 \frac{dV(t)}{dt} = -I(t) - \frac{1}{3}V(t) + \frac{1}{3}V_s(t) + 0.2 \frac{dV_s(t)}{dt}$$

$$\frac{dV_s(t)}{dt} = -10e^{-2t} = -2V_s(t) \text{ 이므로}$$

$$\frac{dV(t)}{dt} = -2I(t) - \frac{2}{3}V(t) + \frac{2}{3}V_s(t) + 0.4(-2V_s(t)) = -2I(t) - \frac{2}{3}V(t) - \frac{2}{15}V_s(t)$$

$$\begin{bmatrix} \frac{dI(t)}{dt} \\ \frac{dV(t)}{dt} \end{bmatrix} = \begin{bmatrix} -10 & 5 \\ -2 & -\frac{2}{3} \end{bmatrix} \begin{bmatrix} I(t) \\ V(t) \end{bmatrix} + \begin{bmatrix} 0 \\ -\frac{2}{15}V_s(t) \end{bmatrix}$$

17. 【정답】 ②

$$\text{특성 임피던스 } Z_0 = \sqrt{\frac{1 \times 10^{-6}}{400 \times 10^{-12}}} = \sqrt{\frac{10^6}{400}} = \sqrt{2500} = 50 [\Omega]$$

$$\text{반사계수 } \rho = \frac{150 - 50}{150 + 50} = \frac{100}{200} = 0.5$$

$$\text{반사파 } V^- = \rho \times 150 = 75 [\text{V}]$$

18. 【정답】 ④

1) $t < 0$

$$50 - 60I(t) - 200I(t) = 0, \quad I(t) = \frac{5}{26} \doteq 0.19 [\text{A}]$$

2) $t \geq 0$

$$t < 0 \text{에서 } \frac{120 - V_a}{10} = \frac{V_a}{50}, \quad V_a = 100 [\text{V}] \text{ 이므로}$$

$$I(0^+) = \frac{100}{200} = 0.5 [\text{A}]$$

$$I(\infty) = \frac{50}{60 + \frac{200 \times 50}{200 + 50}} \times \frac{50}{200 + 50} = \frac{1}{2} \times \frac{1}{5} = 0.1 [\text{A}]$$

따라서 $I(t)$ 로 가장 알맞은 것은 ④번이다.

19. 【정답】 ④

$$R + j\omega L = \overline{R - \frac{j}{\omega C}} = R + \frac{j}{\omega C}$$

$$\omega L = \frac{1}{\omega C}, \quad L = \frac{1}{\omega^2 C}$$

$$\text{이때 최대 전력은 } \left(\frac{\frac{V_m}{\sqrt{2}}}{2R} \right)^2 R = \frac{V_m^2}{8R}$$

20. 【정답】 ①

$$\text{전류를 } I(t) \text{라 하면 } I(t) = C \frac{dV_o}{dt}$$

$$E(t) = RI(t) + V_o(t) = RC \frac{dV_o}{dt} + V_o(t)$$

라플라스 변환하면

$$\frac{A}{s} = RC(sV_o(s) - V_c(0)) + V_o(s)$$

$$(sRC + 1)V_o(s) = \frac{A}{s} + RCV_c(0)$$

$$V_o(s) = \frac{\frac{A}{s} + RCV_c(0)}{sRC + 1} = \frac{A}{s(sRC + 1)} + \frac{RCV_c(0)}{sRC + 1}$$

$$V_o(s) = A \left(\frac{1}{s} - \frac{1}{s + \frac{1}{RC}} \right) + \frac{V_c(0)}{s + \frac{1}{RC}}$$

$$V_o(t) = A \left(1 - e^{-\frac{t}{RC}} \right) u(t) + V_c(0) e^{-\frac{t}{RC}} u(t)$$

$$V_o(t) = Au(t) + (-A + V_c(0)) e^{-\frac{t}{RC}} u(t)$$

① Transient response는 $(-A + V_c(0)) e^{-\frac{t}{RC}} u(t)$ 이다.

② Zero-input response는 $V_c(0) e^{-\frac{t}{RC}} u(t)$ 이다.

③ Steady-state response는 $Au(t)$ 이다.

④ Zero-state response는 $A \left(1 - e^{-\frac{t}{RC}} \right) u(t)$ 이다.