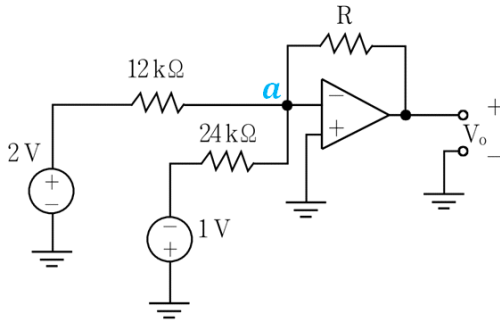


2012년 국가직 7급 회로이론 인책형 해설

01. ④	02. ②	03. ④	04. ①	05. ①	06. ①	07. ③	08. ②	09. ④	10. ④
11. ①	12. ②	13. ②	14. ④	15. ①	16. ①	17. ①	18. ③	19. ③	20. ④

1. 【정답】 ④



$$V_a = 0 \text{ [V]}$$

$$\text{Node a : } \frac{2-0}{12} + \frac{-1-0}{24} = \frac{0-(-6)}{R}$$

$$\frac{1}{8} = \frac{6}{R}, R = 48 \text{ [}\Omega\text{]}$$

2. 【정답】 ②

$$R_{eq} = 5 \text{ [k}\Omega\text{]} \text{ 이므로 } \tau = R_{eq}C = 5 \times 10^3 \times 2 \times 10^{-6} = 10^{-2} \text{ [sec]} = 10^3 \text{ [msec]}$$

3. 【정답】 ④

부하에서 소비되는 전력이 최대일 때이므로

$$Z_L = \overline{Z_t} = 10 - j10$$

$$P_{\max} = \frac{V_t^2}{4R} = \frac{50^2}{10} = 250 \text{ [W]}$$

4. 【정답】 ①

$$H(s) = \frac{10^4(s+1)}{(s+10)(s+100)} = \frac{10^4(s+1)}{10^3\left(\frac{s}{10}+1\right)\left(\frac{s}{100}+1\right)} = \frac{10(s+1)}{\left(\frac{s}{10}+1\right)\left(\frac{s}{100}+1\right)}$$

$$\omega < 1 \text{ 일 때 기울기 } 0 \text{ 이고 } 20\log|H(j\omega)| = 20\log 10 = 20 \text{ [dB]}$$


$$1 \leq \omega < 10 \text{ 일 때 기울기 } +20$$

$$10 \leq \omega < 100 \text{ 일 때 기울기 } +20 - 20 = 0$$

$$\omega \geq 100 \text{ 일 때 기울기 } +20 - 20 - 20 = -20$$

따라서 보드 선도의 크기로 가장 적절한 것은 ①번이다.

5. 【정답】 ①

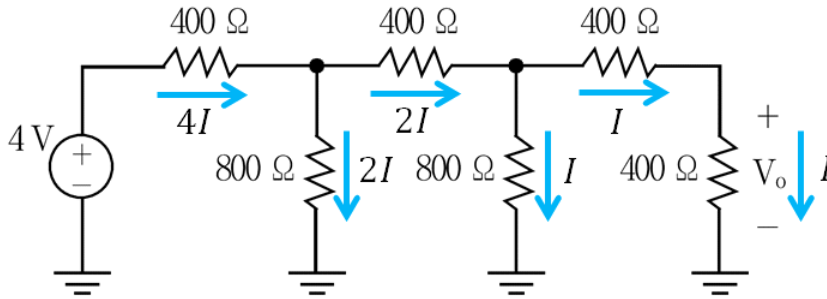

$$I = \frac{4}{400 \times 4 + 800 \times 2} = \frac{4}{3200} = \frac{1}{800} \text{ [A]}$$

$$V_o = 400 \times \frac{1}{800} = 0.5 \text{ [V]}$$

6. 【정답】 ①

$$Y_{eq} = 0.1j\omega + \frac{1}{10} + \frac{1}{2j\omega + 2} = 0.1 + 0.1j\omega + \frac{1 - j\omega}{2(\omega^2 + 1)}$$

어드미턴스의 허수부가 없어야 하므로

$$0.1\omega = \frac{\omega}{2(\omega^2 + 1)}, \quad 0.2(\omega^2 + 1) = 1$$

$$\omega = 2 \text{ [rad/s]}$$

7. 【정답】 ③

$$\frac{v_1 - v_2}{2} = v_2 + \frac{dv_2}{dt}, \text{ 라플라스 변환하면 } V_1 - V_2 = 2V_2 + 2sV_2$$

$$\frac{v_1 - v_2}{2} = -\frac{dv_1}{dt}, \text{ 라플라스 변환하면 } V_1 - V_2 = -2(sV_1 - 1)$$

$$V_1 = (2s + 3)V_2, \quad (2s + 1)V_1 = V_2 + 2$$

$$V_2(s) = \frac{2}{(2s + 3)(2s + 1) - 1} = \frac{2}{4s^2 + 8s + 2} = \frac{1}{2s^2 + 4s + 1}$$

8. 【정답】 ②

$$V_1 = \frac{100}{\sqrt{2}} \angle 0^\circ, \quad V_2 = \frac{40}{\sqrt{2}} \angle 0^\circ, \quad V_3 = \frac{30}{\sqrt{2}} \angle 90^\circ$$

$$I_1 = \frac{10}{\sqrt{2}} \angle -60^\circ, \quad I_2 = 0, \quad I_3 = \frac{2}{\sqrt{2}} \angle 30^\circ$$

$$P = \left(\frac{100}{\sqrt{2}} \right) \left(\frac{10}{\sqrt{2}} \right) \cos 60^\circ + \left(\frac{30}{\sqrt{2}} \right) \left(\frac{2}{\sqrt{2}} \right) \cos 60^\circ = 250 + 15 = 265 \text{ [W]}$$

9. 【정답】 ④

$$2 + 1 + I = 0, \quad I = -3 \text{ [A]}$$

$$V_1 = 3I - 2I = I = -3 \text{ [V]}$$

10. 【정답】 ④

$$V(s) = \frac{1}{s^2}$$

$$I(s) = \frac{V(s)}{Z(s)} = \frac{\frac{1}{s^2}}{0.5s + 1 + \frac{1}{s}} = \frac{1}{0.5s^3 + s^2 + s} = \frac{2}{s(s^2 + 2s + 2)}$$

11. 【정답】 ①


$$i_1(0+) = \frac{V}{R_1}, \quad i_2(0+) = 0$$

$$i_1(0+) + i_2(0+) = \frac{V}{R_1}$$

12. 【정답】 ②

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{I_1 + \frac{2}{s}I_1}{I_1} = 1 + \frac{2}{s}$$

13. 【정답】 ②

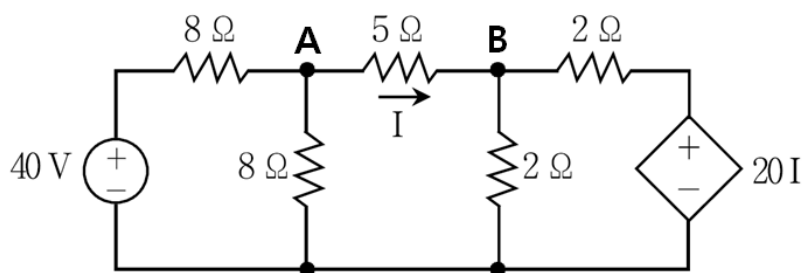


$$\text{노드 A : } \frac{40 - V_A}{8} = \frac{V_A}{8} + I, \quad V_A = 20 - 4I$$

$$\text{노드 B : } I = \frac{V_B}{2} + \frac{V_B - 20I}{2}, \quad V_B = 11I$$

$$20 - 4I - 11I = 5I, \quad I = 1 \text{ [A]}$$

$$P = 1^2 \cdot 5 = 5 \text{ [W]}$$

14. 【정답】 ④

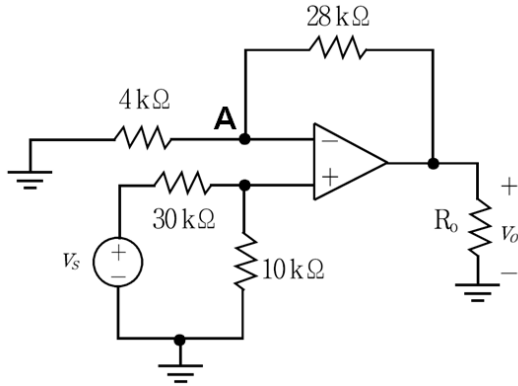

$$\frac{v_o - v_A}{28} = \frac{v_A}{4}, \quad v_o = 8v_A$$

$$\frac{v_s - v_A}{30} = \frac{v_A}{10}, \quad v_s = 4v_A$$

$$\frac{v_o}{v_s} = \frac{8v_A}{4v_A} = 2, \quad v_o = 2v_s \text{ [A]}$$

위상이 변하지 않으므로 비반전증폭기이며 $v_o = 2v_s$ [A] 이다.

15. 【정답】 ①

① 공진 각주파수 ω_0 는 어드미턴스의 허수부가 0일 때 발생한다.

16. 【정답】 ①

$$H(s) = \frac{I_o(s)}{V_i(s)} = \frac{\frac{1}{0.25s}}{4 + \frac{1}{0.25s}} \cdot \frac{1}{1 + 2s + \frac{\frac{4}{0.25s}}{4 + \frac{1}{0.25s}}} = \frac{1}{s+1} \cdot \frac{1}{1 + 2s + \frac{4}{s+1}}$$

$$H(s) = \frac{1}{s+1} \cdot \frac{s+1}{(1+2s)(s+1)+4} = \frac{1}{2s^2+3s+5}$$

17. 【정답】 ①

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{(R_1 + R_2)I_1}{I_1} = R_1 + R_2$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{0}{V_2}$$

$$V_2 = 0 \text{ 일 때 } V_2 = AV_s + I_2 R_3 = 0, \quad I_2 = -A \frac{V_s}{R_3} = -A \frac{I_1 R_2}{R_3}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \frac{-A \frac{I_1 R_2}{R_3}}{I_1} = -A \frac{R_2}{R_3}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{I_2}{I_2 R_3} = \frac{1}{R_3}$$

18. 【정답】 ③

내전압이 작은 쪽이 먼저 파괴되므로 작은 쪽을 기준으로 한다.

$$C_2 + C_3 = 10 + 6 = 16 \text{ [mF]}$$

$$C_1 : (C_2 + C_3) = 20 : 16 = 5 : 4 \text{ 이므로 } V_1 : V_2 = 4 : 5$$

$$V_2 = \frac{5}{4} V_1 = \frac{5}{4} \times 50 = 62.5 \text{ [V]}$$

$$\text{따라서 최대 전압은 } 50 + 62.5 = 112.5 \text{ [V]}$$

19. 【정답】 ③

$$N_1 : N_2 = 2 : 1 \text{ 이므로 } V_1 : V_2 = 2 : 1, \quad I_1 : I_2 = 1 : 2 \text{ 이다.}$$

$$120 \angle 0^\circ = \left(4 + \frac{1}{j0.25} \right) I_1 + V_1$$

$$V_1 = 2V_2 = 2(2 + j)I_2 = 4(2 + j)I_1$$

$$120 \angle 0^\circ = (4 - j4)I_1 + (8 + j4)I_1 = 12I_1$$

$$I_1 = \frac{120 \angle 0^\circ}{12} = 10 \angle 0^\circ$$

20. 【정답】 ④

$$R_{Th} = \frac{2 \times 2}{2 + 2} + 4 = 5 \text{ [}\Omega\text{]} \text{ 이므로 } \tau = R_{Th} C = 5 \times 0.4 = 2 \text{ [sec]}$$

$$v_0(0^-) = 2 \text{ [V]}, \quad v_0(\infty) = 5 \text{ [V]} \text{ 이므로}$$

$$v_0(t) = 5 + (2 - 5)e^{-t/2} = 5 - 3e^{-0.5t} \text{ [V]}$$