

2014년 국가직 7급 회로이론 A책형 해설

01. ②	02. ①	03. ①	04. ③	05. ②	06. ②	07. ②	08. ③	09. ②	10. ④
11. ①	12. ③	13. ④	14. ③	15. ③	16. ①	17. ④	18. ③	19. ④	20. ②

1. 【정답】 ②

$$Z_{eq} = 2 + j2 + \frac{1}{j2 \times \frac{1}{4}} = 2 + j2 + \frac{2}{j} = 2 + j2 - j2 = 2 \text{ [}\Omega\text{]}$$

2. 【정답】 ①

$$I(s) = \frac{s}{2s+s} \cdot \frac{3}{s^2} = \frac{1}{s^2} \text{ 이므로 역변환하면 } i(t) = t \text{ [A]}$$

3. 【정답】 ①

$$\text{교류 전압원의 실효값 } \frac{20}{\sqrt{2}} = 10\sqrt{2} \text{ [V] 이므로}$$

$$\text{저항 } R \text{에 전달되는 평균전력 } P = \frac{10^2}{5} + \frac{(10\sqrt{2})^2}{5} = 20 + 40 = 60 \text{ [W]}$$

4. 【정답】 ③

$$Z(s) = \frac{\frac{2}{s}}{2 + \frac{1}{s}} + 2s = \frac{2}{2s+1} + 2s = \frac{2+2s(2s+1)}{2s+1} = \frac{4s^2+2s+2}{2s+1}$$

$$\text{극점 } p = -\frac{1}{2}$$

$$4s^2 + 2s + 2 = 0, \quad 2s^2 + s + 1 = 0$$

$$s = \frac{-1 \pm \sqrt{1^2 - 4 \cdot 2 \cdot 1}}{4} = -\frac{1}{4} \pm j\frac{\sqrt{7}}{4}$$

$$\text{영점 } z_1, z_2 = -\frac{1}{4} \pm j\frac{\sqrt{7}}{4}$$

5. 【정답】 ②

$$I(s) = \frac{20}{20+30+\frac{1}{10^{-4}s}} \cdot \frac{7.5}{s} = \frac{2 \times 10^{-3}s}{5 \times 10^{-3}s+1} \cdot \frac{7.5}{s}$$

$$I(s) = \frac{15 \times 10^{-3}}{5 \times 10^{-3}s + 1} = \frac{3}{s + 200} \text{이므로 역변환하면 } i(t) = 3e^{-200t} [\text{mA}]$$

6. 【정답】 ②

$$\frac{\frac{V_i - 0}{1}}{0.005 \times 10^{-6}s} = \frac{0 - V_o}{20 \times 10^3}$$

$$5 \times 10^{-9}s V_i = -5 \times 10^{-5} V_o, \quad V_o = -10^{-4}s V_i$$

$$\text{역변환하면 } v_i(t) = -10^{-4} \frac{dv_i}{dt}$$

$$0 \sim 1 \mu s \text{에서 } \frac{dv_i}{dt} = \frac{0.1}{10^{-6}} = 10^5 [\text{V/s}] \text{이므로 } v_i(t) = -10 [\text{V}] \text{이다.}$$

$$1 \sim 3 \mu s \text{에서 } \frac{dv_i}{dt} = -\frac{0.1}{10^{-6}} = -10^5 [\text{V/s}] \text{이므로 } v_i(t) = 10 [\text{V}] \text{이다.}$$

따라서 보기 중 가장 적절한 그래프는 ②번이다.

7. 【정답】 ②

2차측 부하저항 $10 [\Omega]$ 에 최대전력을 전달해야하므로 1차측의 임피던스는 태브넨 등가저항인 $Z_1 = R_{Th} = 1 [\text{k}\Omega]$ 이다.

$$\frac{Z_1}{Z_2} = \left(\frac{n_1}{n_2} \right)^2 \text{에서 } \frac{n_1}{n_2} = \sqrt{\frac{10^3}{10}} = 10, \quad n_1 : n_2 = 10 : 1$$

$$\frac{v_1}{n_1} = \frac{v_2}{n_2} \text{에서 } v_1 = \frac{v_i}{2} \text{이므로 부하에서 소비되는 전력}$$

$$P = \frac{v_2^2}{10} = \frac{\left(\frac{n_2}{n_1} v_1 \right)^2}{10} = \left(\frac{n_2}{n_1} \right)^2 \frac{\left(\frac{v_i}{2} \right)^2}{10} = \frac{1}{10^2} \frac{v_i^2}{40} = \frac{v_i^2}{4000} \text{이다.}$$

8. 【정답】 ③

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{\frac{8}{s}}{4 + \frac{2}{s}}}{2s + \frac{\frac{8}{s}}{4 + \frac{2}{s}}} = \frac{\frac{8}{s}}{2s \left(4 + \frac{2}{s} \right) + \frac{8}{s}} = \frac{8}{2s(4s + 2) + 8} = \frac{8}{8s^2 + 4s + 8}$$

$$H(s) = \frac{2}{2s^2 + s + 2}$$

9. 【정답】 ②

$$v_i(t) = u(t-1) + u(t-2) - 2u(t-3)$$

$$V_i(s) = \frac{1}{s}e^{-s} + \frac{1}{s}e^{-2s} - \frac{2}{s}e^{-3s} = \frac{1}{s}(e^{-s} + e^{-2s} - 2e^{-3s})$$

$$I(s) = \frac{V_i(s)}{1+s} = \frac{1}{s(s+1)}(e^{-s} + e^{-2s} - 2e^{-3s})$$

$$I(s) = \left(\frac{1}{s} - \frac{1}{s+1} \right) (e^{-s} + e^{-2s} - 2e^{-3s})$$

10. 【정답】 ④

먼저 $0 \leq t < 0.25$ [s] 에서 $\frac{L}{R} = \frac{1+1}{1+1} = 1$ 이므로

$$i(t) = 10 + (0 - 10)e^{-t} = 10(1 - e^{-t}) \text{ 이다.}$$

스위치를 b 에 연결하면 b 의 전위는 10 [V] 이므로 폐회로에 키르히호프 법칙을 적용하면

$$10 - i(t) - \frac{di}{dt} - 3i(t) = 0, \quad \frac{di}{dt} + 4i(t) = 10$$

$$i(0.25) = 10(1 - e^{-0.25}), \quad i(\infty) = 0 \text{ 이므로 } i(t) = 0 + 10(1 - e^{-0.25})e^{-4(t-0.25)}$$

$$i(t) = 10e(1 - e^{-0.25})e^{-4t} = 10(e - e^{0.75})e^{-4t}$$

11. 【정답】 ①

도트가 같은 방향이므로

$$v_1 = L \frac{di_1}{dt} + M \frac{di_2}{dt}, \quad v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \text{ 이다.}$$

12. 【정답】 ③

$$Z = 10 + j \left(2\pi \times 50 \times \frac{1}{10\pi} \right) = 10 + j10$$

$$\text{따라서 역률(power factor)} \quad \frac{10}{10\sqrt{2}} = \frac{1}{\sqrt{2}} = \frac{\sqrt{2}}{2}$$

13. 【정답】 ④

$$Z_{11} = \frac{V_1}{I_1} \bigg|_{I_2=0} = \frac{4I_1}{I_1} = 4, \quad Z_{12} = \frac{V_1}{I_2} \bigg|_{I_1=0} = \frac{I_2}{I_2} = 1$$

$$Z_{21} = \frac{V_2}{I_1} \bigg|_{I_2=0} = \frac{I_1}{I_1} = 1, \quad Z_{22} = \frac{V_2}{I_2} \bigg|_{I_1=0} = \frac{(s+1)I_2}{I_2} = s+1$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 4 & 1 \\ 1 & s+1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

14. 【정답】 ③

$$\frac{V_o(s)}{V_i(s)} = \frac{10}{\frac{1}{sC} + sL + 10} = \frac{10Cs}{LCs^2 + 10Cs + 1} = \frac{\frac{10}{L}s}{s^2 + \frac{10}{L}s + \frac{1}{LC}}$$

$$\frac{10}{L} = 5, \quad \frac{1}{LC} = 10$$

$$L = 2, \quad C = \frac{1}{20} = 0.05$$

15. 【정답】 ③

$$\text{입력의 라플라스 변환 : } \frac{1}{s}$$

$$\text{출력의 라플라스 변환 : } 10 \frac{s}{s^2 + 2^2} = \frac{10s}{s^2 + 4}$$

$$H(s) = \frac{\frac{10s}{s^2 + 4}}{\frac{1}{s}} = \frac{10s^2}{s^2 + 4}$$

16. 【정답】 ①

$$R_n = R_{Th} = 4 \parallel (7+5) = \frac{4 \times 12}{4+12} = 3 \, [\Omega]$$

$$2 = \frac{7I_{sc} - 10}{5} + I_{sc}, \quad 12I_{sc} = 20, \quad I_{sc} = \frac{20}{12} = \frac{5}{3} \, [A]$$


17. 【정답】 ④

$$V = \frac{2}{\sqrt{2}} \angle \frac{\pi}{6} = \sqrt{2} \angle \frac{\pi}{6} \text{이다.}$$

$$I = \frac{\sqrt{2} \angle \frac{\pi}{6}}{2 + j2} = \frac{\sqrt{2} \angle \frac{\pi}{6}}{2\sqrt{2} \angle \frac{\pi}{4}} = \frac{1}{2} \angle \left(\frac{\pi}{6} - \frac{\pi}{4} \right) = \frac{1}{2} \angle -\frac{\pi}{12}$$

$$\text{따라서 } i(t) = \frac{\sqrt{2}}{2} \sin\left(2t - \frac{\pi}{12}\right) = \frac{1}{\sqrt{2}} \sin\left(2t - \frac{\pi}{12}\right)$$

18. 【정답】 ③

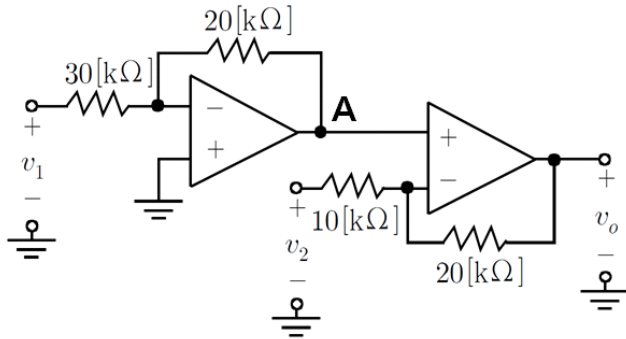


$$\frac{v_1 - 0}{30} = \frac{0 - v_A}{20}, \quad v_A = -\frac{2}{3}v_1$$

$$\frac{v_A - v_2}{10} = \frac{v_o - v_A}{20}, \quad v_o = 2(v_A - v_2) + v_A$$

$$v_o = 2\left(-\frac{2}{3}v_1 - v_2\right) - \frac{2}{3}v_1 = -2v_1 - 2v_2$$

19. 【정답】 ④

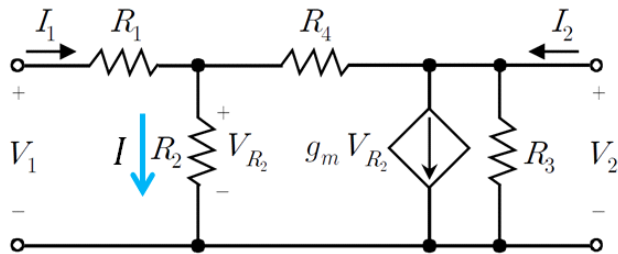

$V_{R_2} = IR_2$ 이고, 저항 R_3 에 흐르는 전류를 I_3 라 하면

$$I_2 = I_3 + I + g_m V_{R_2} = I_3 + I + g_m R_2 I = I_3 + (g_m R_2 + 1)I$$

$$I_3 = \frac{V_2}{R_3} \text{이고 } V_2 = I(R_2 + R_4) \text{이므로}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{I_3 + (g_m R_2 + 1)I}{V_2} = \frac{1}{R_3} + \frac{(g_m R_2 + 1)I}{i(R_2 + R_4)} = \frac{1}{R_3} + \frac{g_m R_2 + 1}{R_2 + R_4}$$

20. 【정답】 ②

$$Z(j\omega) = 2 + \frac{j2\left(1 + \frac{1}{j}\right)}{j2 + 1 + \frac{1}{j}} = 2 + \frac{j2(1-j)}{1+j} = 2 + j(1-j)^2 = 4$$

$$P = \frac{\left(\frac{4}{\sqrt{2}}\right)^2}{4} = 2 \text{ [W]}$$